
### **COMPONENT:**


- 1. Arduino Uno R3
- 2. L298 Motor Driver
- 3. DC motor
- 4. HC-05 Bluetooth Module
- 5. Infrared IR Wireless
- 6. Remote Control Module
- 7. IR Sensor
- 8. Ultrasonic Sensor Holder
- 9. Servo Motor
- 10. Ultrasonic Sensor hc-sr0
- 11. Jumper Wires
- 12. LED
- 13. LM358 Dual Operational Amplifier
- 14. 10k Variable Resistor
- 15. BD139 NPN Transistor
- 16.4148 Diode
- 17. LDR Sensor
- 18. Resistor
- 19. Capacitor
- 20. TIP32C Transistor
- 21. 18650 3.7V 1200mAh Lithium-Ion Rechargeable Cell
- 22. On/Off switch

### **BLOCK DIAGRAM:**


### 1) Line Following

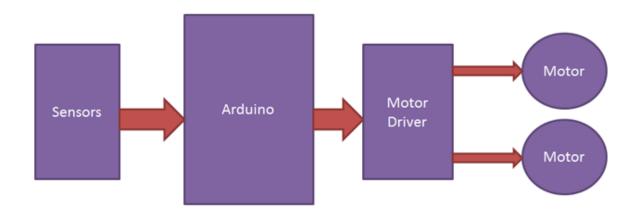


# 2) Obstacle Avoiding

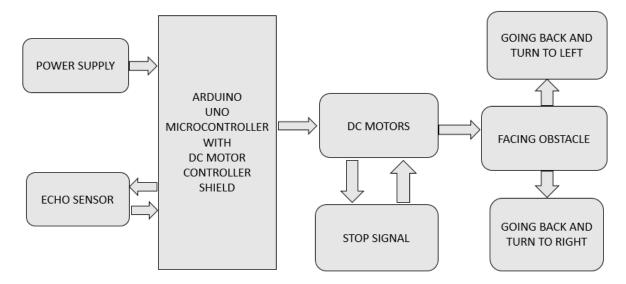


# 3) Voice Control

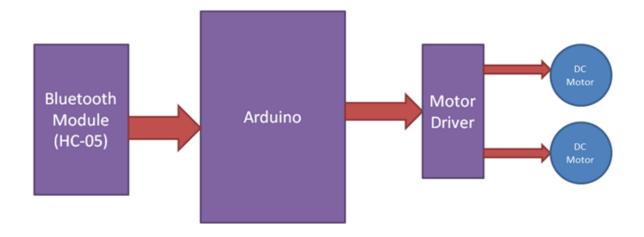

# 4) Light Following

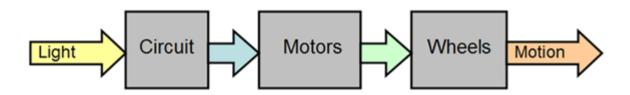

### 5) Human Following

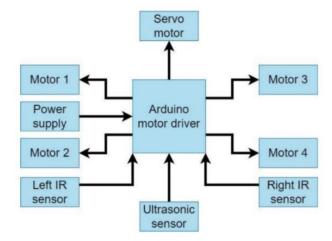

### **CONNECTION:**

1) Connect L298 Motor Driver to Arduino UNO:

| Arduino UNO | L298 Motor Driver |
|-------------|-------------------|
| D10         | ENA               |
| D9          | IN1               |
| D8          | IN2               |
| D7          | IN3               |
| D6          | IN4               |
| D5          | ENB               |
| GND         | GND               |
| VCC=5V      | VCC=12V           |

## 2) Connect L298 Motor Driver to DC motor:

| L298 Motor Driver | DC motor          |                |
|-------------------|-------------------|----------------|
| OUT 1             | Positive terminal | DC motor 1 & 2 |
| OUT2              | Negative terminal |                |
| OUT3              | Positive terminal | DC motor 3 & 4 |
| OUT4              | Negative terminal |                |

Notes: We will connect the motors in criss cross pattern. This is because we have to make the car in such a way that two side motor rotates in same direction in order to go Forward Backward and other known directions

# 3) Connect IR Sensors for line following to Arduino UNO:

| IR Sensors             | Arduino UNO |
|------------------------|-------------|
| Out IR Sensors (Right) | A0          |
| Out IR Sensors (Left)  | A1          |
| GND                    | GND         |
| VCC                    | VCC         |

# 4) Connect IR Sensors for human following to Arduino UNO:

| IR Sensors | Arduino UNO |
|------------|-------------|
| Out        | A5          |
| GND        | GND         |
| VCC        | VCC         |

### 5) Connect Ultrasonic sensor to Arduino UNO:

| Ultrasonic sensor | Arduino UNO |
|-------------------|-------------|
| Trig              | A3          |
| Echo              | A2          |
| GND               | GND         |
| VCC               | VCC         |


# 6) Connect Bluetooth Module to Arduino UNO:


| Bluetooth Module | Arduino UNO |
|------------------|-------------|
| Rx               | D3          |
| Tx               | D2          |
| GND              | GND         |
| VCC              | VCC         |

# 7) Connect Servo motor to Arduino UNO:

| Servo motor | Arduino UNO |
|-------------|-------------|
| Out         | A4          |
| GND         | GND         |
| VCC         | VCC         |

# 8) Connection of Light following robot

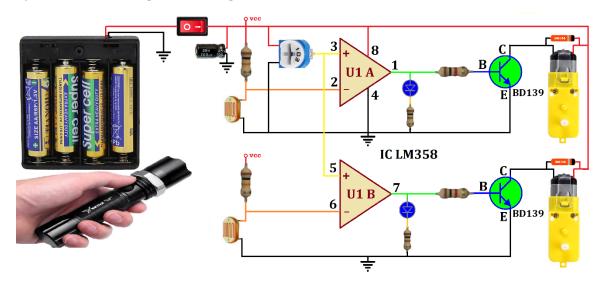

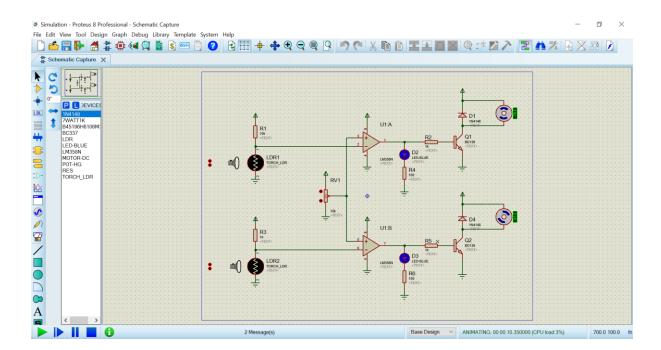

Notes: Simulation file is attachment on this link: - <a href="https://drive.google.com/file/d/18aImWSFfpM8N7vFQDc9QKJYZe7oOsKI/view?usp=sharing">https://drive.google.com/file/d/18aImWSFfpM8N7vFQDc9QKJYZe7oOsKI/view?usp=sharing</a>

## **SOFTWARE UESD:**

- I. Proteus 8<sup>TM</sup> software
- II. Arduino IDE
- III. Easy EDA